

# FINAL EXAM: POWER SYSTEM PROTECTION AND CONTROL (EE4040)

**Duration: 90 minutes – Open book exam**

**No. 01**

**Student name:**

**Signature:**


**Student ID:**

**Question 1:** Explain meaning of voltage transformer's specification (1 point):

Voltage level (V)	Total core	Core 1	Core 2 & Core 3
$\frac{115000}{\sqrt{3}} : \frac{100}{\sqrt{3}} : \frac{100}{\sqrt{3}} : \frac{100}{\sqrt{3}}$	3	100VA; 0,2	200VA; 3P

**Question 2:** Calculate setting values for overcurrent protection of 110kV transformer:


Transformer rated power: 32 MVA					
Voltage level $U_1/U_2/U_3$ (kV): 110/23/35					
Permissible overload factor: 1,2					
Current measured by $BI_1$ when fault occurs at N3 (kA)					
$N^{(3)}$			$N^{(2)}$		
1,47			1,27		
Current measured by $BI_1$ when fault occurs at N2 (kA)					
$N^{(3)}$	$N^{(2)}$	$N^{(1)}$	$N^{(1,1)}$	$3I_0$ fault type $N^{(1)}$	$3I_0$ fault type $N^{(1,1)}$
2,37	1,93	2,15	2,25	1,68	1,47

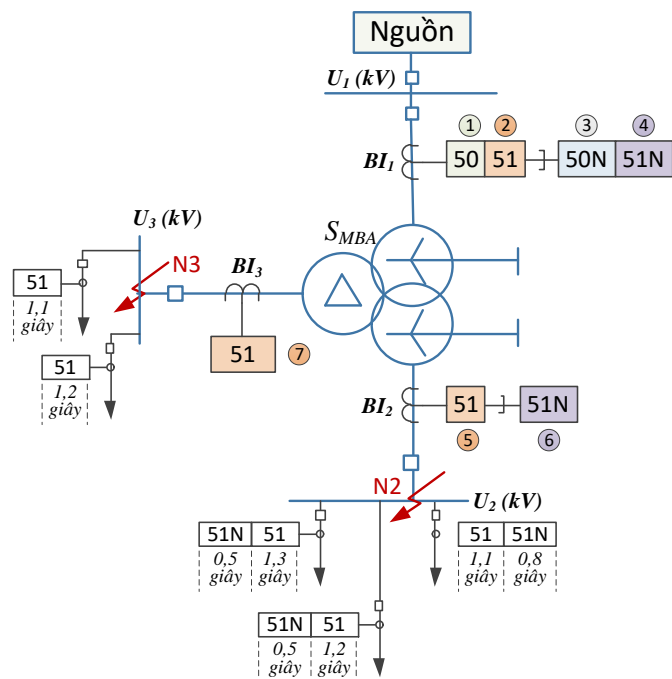

**Require:**

- Determine current transformer ratios for  $BI_1$ ;  $BI_2$ ;  $BI_3$  (0,5 point)  
(Rated primary current of BI can be chosen as: 10 - 12,5 - 15 - 20 - 25 - 30 - 40 - 50 - 60 - 75A and its multiple of 10, 100, 1000 times).
- Calculate pickup current and time delay for relay 2 & 3 (1 point)
- Evaluate minimum sensitivity of relay 2? Determine if this sensitivity of relay 2 meets regulation or not (0,5 point)?

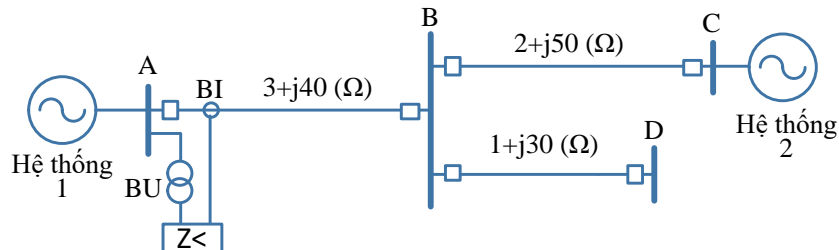
**Question 3:** Calculate setting values for distance protection in following scheme:



Network rated voltage: 115kV

- Calculate setting values for 3 protection zones of distance protection (1,5 point)
- Assume that maximum line load is 300MVA with power factor  $\cos\varphi=0.85$ . Determine maximum resistive reach value of protection zone (1,5 point)

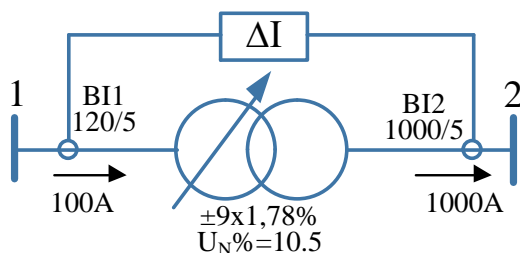**Question 4:** Consider following differential protection scheme:



Given data:

- Rated current of side 1 is 100 (A) ; CT ratio (BI1) is 120/5
- Rated current of side 2 is 1000 (A) ; CT ratio (BI2) is 1000/5
- Maximum CT ratio error is 10%
- Voltage regulation range of transformer:  $\pm 9 \times 1,78\%$
- Short-circuit voltage (percent)  $U_N\%=10,5$

**Require:**

- Evaluate maximum bias current during normal operation of transformer with permissible overload factor of 120% (1 point).
- If differential relay is has ability to compensate for current transformer ratio at both side then what could be value of that bias current? (1 point)?
- Determine minimum low-set value of differential relay characteristic (in per unit of  $I_{\text{secondary CT}}=5A$ )? (1 point);
- If high-set value of differential relay characteristic is 10 (in per unit of transformer rating current) then what could be minimum short-circuit voltage value of transformer? (1 point)

## FINAL EXAM: POWER SYSTEM PROTECTION AND CONTROL (EE4040)

### SOLUTION

**Question 1:** Explain meaning of voltage transformer's specification (1 point):


Voltage level (V)	Total core	Core 1	Core 2 & Core 3
$\frac{115000}{\sqrt{3}} : \frac{100}{\sqrt{3}} : \frac{100}{\sqrt{3}} : \frac{100}{\sqrt{3}}$	3	100VA; 0,2	200VA; 3P

**Answer:**

- This voltage transformer can be installed in 110kV network
- It has three cores with secondary voltage of 100V
- Core 1 has accuracy class of 0,2 and rated power of 100VA. This core is used for precise metering purpose only.
- Core 2 & Core 3: both have accuracy class of 3P with rated power of 200VA. Both cores are used for protective relaying purpose; not suitable to use for metering due to low accuracy.

**Question 2:** Calculate setting values for overcurrent protection of 110kV transformer:

Transformer rated power: 32 MVA					
Voltage level $U_1/U_2/U_3$ (kV): 110/23/35					
Permissible overload factor: 1,2					
Current measured by $BI_1$ when fault occurs at N3 (kA)					
$N^{(3)}$			$N^{(2)}$		
1,47			1,27		
Current measured by $BI_1$ when fault occurs at N2 (kA)					
$N^{(3)}$	$N^{(2)}$	$N^{(1)}$	$N^{(1,1)}$	$3I_0$ của $N^{(1)}$	$3I_0$ của $N^{(1,1)}$
2,37	1,93	2,15	2,25	1,68	1,47

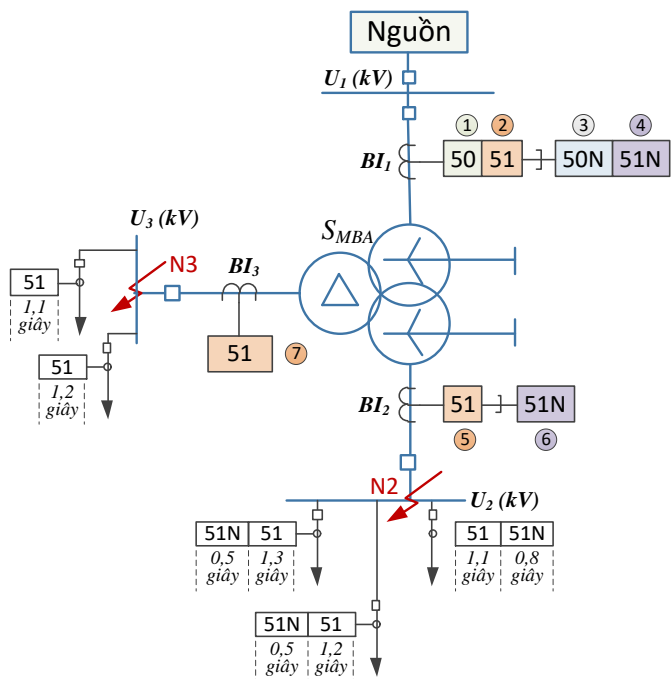

**Require:**

- a. Determine current transformer ratios for BI1; BI2; BI3 (0,5 point)  
(Rated primary current of BI can be chosen as: 10 - 12,5 - 15 - 20 - 25 - 30 - 40 - 50 - 60 - 75A and its multiple of 10, 100, 1000 times).
- b. Calculate pickup current and time delay for relay 2 & 3 (1 point)

- c. Evaluate minimum sensitivity of relay 2? Determine if this sensitivity of relay 2 meets regulation or not (0,5 point)?

**Answer:**

- a. Determine current transformer ratios for BI1; BI2; BI3 (0,5 point)

Rated current of transformer is calculated based on following formula:

$$I_{rated} = \frac{S_{rated}}{\sqrt{3} * U_{rated}}$$

Consider permissible overload factor ( $K_{overload}$ ) then maximum current will be calculated as:

$$I_{max} = K_{overload} * \frac{S_{rated}}{\sqrt{3} * U_{rated}}$$

One should select rated primary current of BI to be equal or greater than  $I_{max}$  and be closet to standard value of manufacture. Secondary currents are all to be 1A.

Results:

Side	$U_{rated}$ (kV)	$S_{rated}$ (MVA)	$I_{rated}$ (kA)	$I_{max}$ (kA)	$I_{BI}$ (A)	Ratio
1	110	32	0.168	0.20	200	<b>200/1</b>
2	23	32	0.803	0.964	1000	<b>1000/1</b>
3	35	32	0.528	0.633	750	<b>750/1</b>

- b. Calculate pickup current and time delay for relay 2 & 3 (1 point)

- Pickup current of time delay overcurrent 2 (ANSI 51):

$$I_{pickup} = K * I_{rated}$$

Minimum value of K can be chosen as 1.5 or higher.

Assume that K=1.6

$$I_{pickup \text{ Relay } 2} = 1.6 * 0.168 = \mathbf{0.269 \text{ (kA)}}$$

Time delay of Relay 5:

$$t_{Relay \ 5} = \max(t_{lines \ 23kV}) + \Delta t = 1.3 + 0.5 = 1.8 \text{ (sec)}$$

(one may select  $\Delta t=0.3 \div 0.6 \text{ sec}$ )

Time delay of Relay 2:

$$t_{Relay \ 2} = t_{Relay \ 5} + \Delta t = 1.8 + 0.5 = \mathbf{2.3 \text{ (sec)}}$$

Alternative: Or student may use more detailed formula:

$$I_{pickup} = \frac{K_{at} * K_{mm}}{K_{tv}} * I_{max}$$

- Pickup current of instantaneous earth fault overcurrent 3 (ANSI 50N):

$$I_{pickup\ Relay\ 3} = K_{at} * 3I_{0\ max\ through\ BI1}$$

Here safety factor  $K_{at}$  can be in range of  $1,1 \div 1,3$

Assume that  $K_{at}=1,1$  hence:

$$I_{pickup\ Relay\ 3} = 1.1 * 1.68 = \mathbf{1.85\ (kA)}$$

Time delay of Relay 3:  $t_{Relay\ 3} = \mathbf{0.05\ (sec)}$


- c. Evaluate minimum sensitivity of relay 2? Determine if this sensitivity of relay 2 meets regulation or not (0,5 point)?

Minimum sensitivity value of relay 2:

$$K_{n\ min} = \frac{I_{short\ circuit\ min\ through\ BI1}}{I_{pickup\ Relay\ 2}} = \frac{1.27}{0.269} = \mathbf{4.72 > 2}$$

This minimum sensitivity value is greater than 2 then it safely meets regulation.

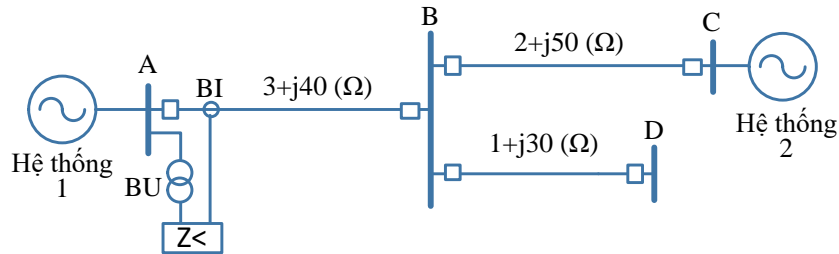**Question 3:** Calculate setting values for distance protection in following scheme:



Network rated voltage: 115kV

- a. Calculate setting values for 3 protection zones of distance protection (1,5 point)

Line AB impedance:  $Z_{line\ AB} = 3 + j40 = 40(86^0) (\Omega)$

Line BC impedance:  $Z_{line\ BC} = 2 + j50 = 50(88^0) (\Omega)$

Line BD impedance:  $Z_{line\ BD} = 1 + j30 = 30(88^0) (\Omega)$

- Setting value for zone I:

$$Z_{pickup\ Zone\ I} = 0.85 * Z_{line\ AB} = 0.85 * 40(86^0) = \mathbf{34(86^0) (\Omega)}$$

(one may select Zone I with setting range of  $(0.8 \div 0.85)$  of  $Z_{line}$ )

Time delay of Zone I:

$$t_{Zone\ I} = \mathbf{0\ (sec)}$$

- Setting value for zone II:

$$\begin{cases} Z_{pickup \text{ Zone II}} \geq 1.2 * Z_{line \text{ AB}} \\ Z_{pickup \text{ Zone II}} \leq Z_{line \text{ AB}} + 0.5 * Z_{shotest \text{ line from bus B}} \end{cases}$$

Hence:

$$Z_{pickup \text{ Zone II}} = 1.2 * (3 + j40) = 3.6 + j48$$

Checking restrain condition:

$$Z_{line \text{ AB}} + 0.5 * Z_{line \text{ BD}} = 3.5 + j55 \rightarrow Z_{pickup \text{ Zone II}} = (3.6 + j48) < (3.5 + j55)$$

Final setting value for Zone II:  $Z_{pickup \text{ Zone II}} = (3.6 + j48) = \mathbf{48.13(86^0)} (\Omega)$

Time delay of Zone II:

$$t_{Zone \text{ II}} = \Delta t = \mathbf{0.5 (sec)}$$

- Setting value for zone III:

$$\begin{aligned} Z_{pickup \text{ Zone III}} &= Z_{line \text{ AB}} + Z_{longest \text{ line from bus B}} = Z_{line \text{ AB}} + Z_{line \text{ BC}} = 5 + j90 \\ &= \mathbf{90.14(87^0)} (\Omega) \end{aligned}$$

Time delay of Zone III:

$$t_{Zone \text{ III}} = 2\Delta t = \mathbf{1.0 (sec)}$$

In practice, time delay of Zone III may be set higher since it may need to coordinate with other protection function.

- Assume that maximum line load is 300MVA with power factor  $\cos\phi=0.85$ . Determine maximum resistive reach value of protection zone (1,5 point)

Rated line voltage is 115kV  $\rightarrow$  minimum allowable operating voltage will be:

$$V_{min} = 85\% * 115\text{kV} = 97.75\text{kV}$$

(one may select value of 90% instead of 85%)

Minimum line load impedance will be:

$$Z_{line \text{ load}} = \frac{V_{min}^2}{S_{load \text{ max}}} = \frac{97.75^2}{300} = 31.85 (\Omega)$$


Power factor  $\cos\phi=0.85$ , hence resistive component of line load impedance will be:

$$R_{line \text{ load}} = \cos\phi * Z_{line \text{ load}} = 27.1 (\Omega)$$

Resistive reach setting of distance relay will be set with margin of 20%, then maximum resistive reach setting could be (one may select different value of margin, but should not be less than 20% due to inherent errors of instrument transformers):

$$R_{reach \text{ max}} = 0.8 * 27.1 = \mathbf{21.68 (\Omega)}$$

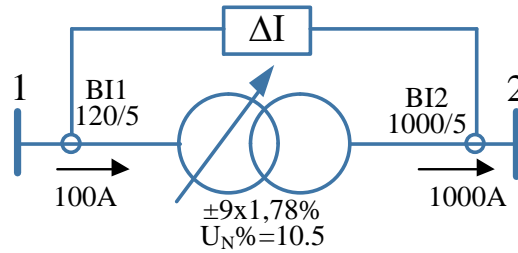**Question 4:** Consider following differential protection scheme:



Given data:

- Rated current of side 1 is 100 (A) ; CT ratio (BI1) is 120/5
- Rated current of side 2 is 1000 (A) ; CT ratio (BI2) is 1000/5
- Maximum CT ratio error is 10%
- Tap changer regulation range:  $\pm 9 \times 1,78\%$
- Short-circuit voltage (percent) :  $U_N\% = 10,5$

**Require:**

a. Evaluate maximum bias current during normal operation of transformer with permissible overload factor of 120% (1 point).

- Maximum secondary current at side 1:  $120\% \times 100A \times \frac{5}{120} = 5A$
- Maximum secondary current at side 2:  $120\% \times 1000A \times \frac{5}{1000} = 6A$
- Bias current due to different current transformer ratio:  $I_{\text{bias CT ratio}} = 6A - 5A = 1A$
- Bias current due to current transformer error and tap changer:

$$I_{\text{bias CT error + tap change}} = 120\% \times 100 \times (10\% + 9 \times 1,78\%) \times \frac{5}{120} = 1.3 A$$

- Total maximum bias current:

$$I_{\text{bias total}} = I_{\text{bias CT ratio}} + I_{\text{bias CT error + tap change}} = 1A + 1.3A = 2.3 A$$

b. If differential relay is has ability to compensate for current transformer ratio at both side then what could be value of that bias current? (1 point)?

If relay has ability to compensate for different current transformer ratio at both side then  $I_{\text{bias CT ratio}}$  will be omitted from total maximum bias current; therefore maximum bias current now only be:  $I_{\text{bias total}} = I_{\text{bias CT error + tap change}} = 1.3 A$

c. Determine minimum low-set value of differential relay characteristic (in per unit of  $I_{\text{secondary CT}} = 5A$ )? (1 point);

Assume that relay has ability to compensate for different current transformer ratio then maximum bias current during normal operation is  $I_{\text{bias total}} = 1.3 A$  as proven in section (b). Low set pickup value of differential relay would not less than:

$$1.3A / 5A = 0.26 \text{ (pu)}$$

Hence one may select setting value of **0.26** or higher but do not greater than 0.5 due to limit in setting range of most of nowadays relays.

- d. If high-set value of differential relay characteristic is 10 (in per unit of transformer rating current) then what could be minimum short-circuit voltage value of transformer? (1 point)

Minimum high set value is set as 120% of  $1/(U_N\%)$

*(one may select value of 100% instead of 120% due to conservative assumption in calculating high set value)*

As high set value is 10 then:

$$U_{N\%} = \frac{1}{10/120\%} * 100 = 12 (\%)$$

----- **END OF SOLUTION** -----